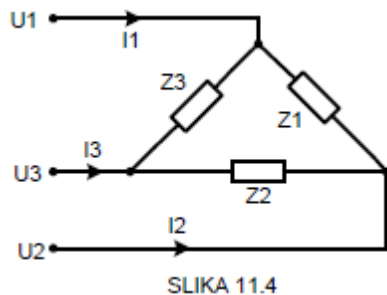


AV-11 Z4, Z5 i Z6 rješenja

AV11-Z4: Na trofaznu mrežu faznih napona $U_f = 3 \times 110 \text{ V}$ priključeno je trošilo spojeno u trokut prema slici 11.4. Impedancije pojedinih grana su: $Z_1 = 14,1 \ \Omega$; $Z_2 = 10 - j10 \ \Omega$; $Z_3 = 10 + j10 \ \Omega$. Odrediti ukupnu radnu snagu P i reaktivnu snagu Q .



Rješenje:

$$\underline{I}_{Z1} = 13.5125 \text{ (A)}; \quad \underline{I}_{Z2} = 3.4869 - j13.0131 \text{ (A)}; \quad \underline{I}_{Z3} = 3.4869 + j13.0131 \text{ (A)}$$

$$P_1 = 2574,5 \text{ (W)}; \quad P_2 = 1815 \text{ (W)}; \quad P_3 = 1815 \text{ (W)}; \quad P = 6204,5 \text{ W}; \quad Q = 0 \text{ (Var)}$$

POSTUPAK:

$$\gg Z_1 = 14.1; \quad Z_2 = 10 - 10*j; \quad Z_3 = 10 + 10*j; \quad U_f = 110;$$

Trošila dobivaju linijski napon:

$$\gg U_L = \sqrt{3} * U_f$$

$$U_L = 190.5256$$

$$\gg U_{12} = U_L * \exp(0*j)$$

$$U_{12} = 190.5256$$

$$\gg U_{23} = U_L * \exp(-2*pi/3*j)$$

$$U_{23} = -9.5263e+01 - 1.6500e+02i$$

$$\gg U_{31} = U_L * \exp(2*pi/3*j)$$

$$U_{31} = -9.5263e+01 + 1.6500e+02i$$

Sada su fazne struje na pojedinim trošilima:

$$\gg I_{1f} = U_{12} / Z_1$$

$$I_{1f} = 13.5125$$

>> I2f=U23/Z2

I2f = 3.4869 -13.0131i = 13,47/-75°

>> I3f=U31/Z3

I3f = 3.4869 +13.0131i = 13,47/75°

Radna snaga je:

>> P1=I1m²*Z1

P1 = 2.5592e+03 W

>> P2=(abs(I2))²*real(Z2)

P2 = 1815 W

>> P3=(abs(I3))²*real(Z3)

P3 = 1815 W

>> P=P1+P2+P3

P = 6.2045e+03 W


Ili preko prividnih snaga:

>> S=U12*conj(I1)+U23*conj(I2)+U31*conj(I3)

S = 6.2045e+03 + 0j VA

Q=0 VAr

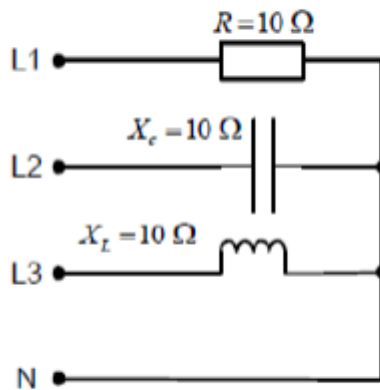AV11-Z5: Potrebno je izračunati struju 0-voda u spoju prema slici 11.5, ako je spoj napajan simetričnim direktnim sustavom napona 3x400 V.



Slika: 11.5

Rješenje:

$$I_0 = 63 \text{ (A)}$$

POSTUPAK:

$$\gg Z1=10; Z2=-10*j; Z3=10*j; UL=400;$$

Trošila dobivaju fazni napon:

$$\gg U_f = UL / \sqrt{3}$$

$$U_f = 230.9401$$

$$\gg U_{f1} = U_f * \exp(0*j)$$

$$U_{f1} = 230.9401 / 0^0$$

$$\gg U_{f2} = U_f * \exp(-2 * \pi / 3 * j)$$

$$U_{f2} = -1.1547e+02 - 2.0000e+02i$$

$$\gg U_{f3} = U_f * \exp(2 * \pi / 3 * j)$$

$$U_{f3} = -1.1547e+02 + 2.0000e+02i$$

Struje trošila su:

$$I1 = U_{f1} / Z1$$

$$I1 = 23.0940 \text{ A}$$

$$\gg I_{z2} = U_{f2} / Z2$$

$$I_2 = 20.0000 - 11.5470i \text{ A}$$

$$\gg I_3 = U_3 / Z_3$$

$$I_3 = 20.0000 + 11.5470i \text{ A}$$


Struja kroz nulvodič je zbroj struja kroz trošila:

$$\gg I_0 = I_1 + I_2 + I_3$$


$$I_0 = 63.0940 \text{ A}$$

$$155.a) \text{ Rješenje: } \bar{I}_0 = \frac{U_1}{10} + \frac{a^2 \cdot U_1}{-j10} + \frac{a \cdot U_1}{j10} = \frac{U_1}{10} \cdot (1 + ja^2 - ja) = 63 \text{ A}; \quad I_0 = 63 \text{ A}$$

Grafičko rješenje:

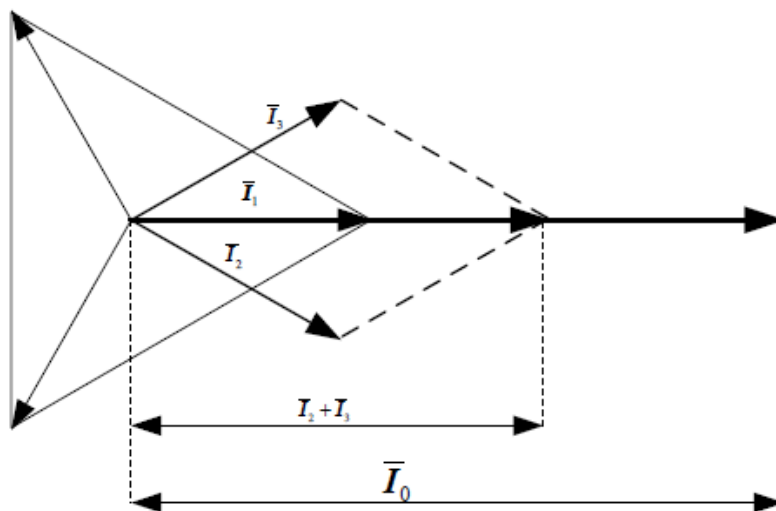

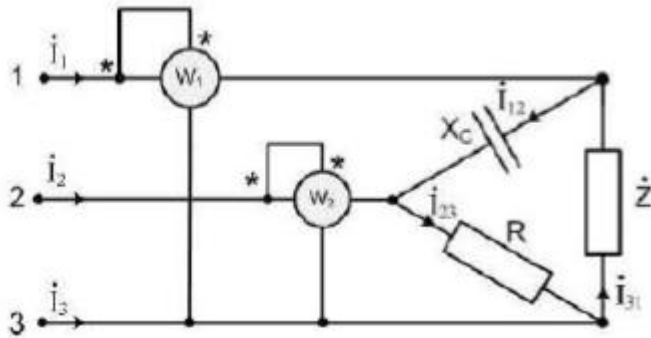AV11-6: U shemi na slici 11.6 treba odrediti što pokazuju vatmetri i izračunati ukupnu radnu snagu sustava. Zadano: $R = 30 \text{ (W)}$, $XC = 30 \text{ (W)}$, $Z = 30/60^\circ \text{ (W)}$ i linijski napon 420 (V).



Slika: 11.6

Rješenje:

$$P_{W1} = -2152 \text{ (W)}; \quad P_{W2} = 10972 \text{ (W)}; \quad P = P_{W1} + P_{W2} = 8820 \text{ (W)}$$

$$\dot{I}_{12} = \frac{\dot{U}_{12}}{-jX_C} = \frac{420|0^\circ}{30|-90^\circ} = 14|90^\circ = j14 \text{ A}$$

$$\dot{I}_{23} = \frac{\dot{U}_{23}}{R} = \frac{420|-120^\circ}{30} = 14|-120^\circ = -7 - j12,124 \text{ A}$$

$$\dot{I}_{31} = \frac{\dot{U}_{31}}{Z} = \frac{420|120^\circ}{30|60^\circ} = 14|60^\circ = 7 + j12,124 \text{ A}$$

$$\dot{I}_1 = \dot{I}_{12} - \dot{I}_{31} = j14 - 7 - j12,124 = 7,247|165^\circ \text{ A}$$

$$\dot{I}_2 = \dot{I}_{23} - \dot{I}_{12} = -7 - j12,124 - j14 = 27,046|255^\circ \text{ A}$$

$$\dot{I}_3 = \dot{I}_{31} - \dot{I}_{23} = 7 + j12,124 + 7 + j12,124 = 28|60^\circ \text{ A}$$

$$P_{W1} = U_{13} \cdot I_1 \cdot \cos \alpha = 420 \cdot 7,247 \cos(-60^\circ - 165^\circ) = -2152 \text{ W}$$

$$P_{W2} = U_{23} \cdot I_2 \cdot \cos \beta = 420 \cdot 27,046 \cos(-120^\circ - 255^\circ) = 10972 \text{ W}$$

$$P = P_{W1} + P_{W2} = 8820 \text{ W}$$

Ili preko prividnih snaga:

$$U_{12} = 420 \cdot \exp(0 \cdot j); \quad U_{23} = 420 \cdot \exp(-2 \cdot \pi / 3 \cdot j); \quad U_{31} = 420 \cdot \exp(2 \cdot \pi / 3 \cdot j)$$

Prvi vatmetar spojen je na linijski napon U_{13} i linijsku struju I_1 pa mjeri realni dio od prividne snage :

$$P_{W1} = \text{real}(U_{13} \cdot I_1^*) = -2152,2 \text{ W}$$

$$U_{13} = 420 \cdot \exp(2 \cdot \pi / 3 \cdot j) \cdot 1 \cdot \exp(-\pi \cdot j)$$

$$U_{13} = 2.1000e+02 - 3.6373e+02i = 420/-60^\circ \text{ V}$$

Vatmetar W2 spojen je na linijski napon U23 i linijsku struju I2 i mjeri realni dio od prividne snage:

$$P_{w2} = \text{real}(U_{23} \cdot \text{conj}(I_2))$$

Gdje je $\text{conj}(I_2)$ konjugirana kompleksna vrijednost od I_2

$$P_{w2} = 10972 \text{ W}$$

Ukupna radna snaga je:

$$\gg P_w = P_{w1} + P_{w2}$$

$$P_w = 8820 \text{ W}$$