

# Z\_5-2kol

Marinko Barukcic, FERIT Osijek

6/6/2016

```
#ZADATAK 05
#Prema sintaksi koristenog softvera veliko ili malo slovo I ('I' ili \
'i') je oznaka imaginarnе jedinice
#Definiranje varijabli za simbolicki izracun, sve su kompleksni \
brojevi osim
var('U_i1','U_i2','U_i3','U','U_00','Z_1','Z_2','Z_3','Z','Z_0','\
U_t1','U_t2','U_t3','I_1','I_2','I_3')
assume(U,'real',Z,'real')
(U_i1, U_i2, U_i3, U, U_00, Z_1, Z_2, Z_3, Z, Z_0, U_t1, U_t2, U_t3, I_1, I_2, I_3)

#Kako je trosilo nesimentricno prvo se odredi napon izmedju \
zvjezdista trosila i izvora
#Ovaj se napon moze odrediti primjenom Millmanovog teorema kao:
U_00=(U_i1/Z_1+U_i2/Z_2+U_i3/Z_3)/(1/Z_1+1/Z_2+1/Z_3+1/Z_0);U_00; \
show('U00= ',U_00)
(U_i1/Z_1 + U_i2/Z_2 + U_i3/Z_3)/(1/Z_0 + 1/Z_1 + 1/Z_2 + 1/Z_3)
U00= 
$$\frac{\frac{U_{i_1}}{Z_1} + \frac{U_{i_2}}{Z_2} + \frac{U_{i_3}}{Z_3}}{\frac{1}{Z_0} + \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$


#Fazni naponi na fazama trosila sada su:
U_t1=U_i1-U_00;show('Ut1= ',U_t1)
Ut1= 
$$U_{i_1} - \frac{\frac{U_{i_1}}{Z_1} + \frac{U_{i_2}}{Z_2} + \frac{U_{i_3}}{Z_3}}{\frac{1}{Z_0} + \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$


U_t2=U_i2-U_00;show('Ut2= ',U_t2)
Ut2= 
$$U_{i_2} - \frac{\frac{U_{i_1}}{Z_1} + \frac{U_{i_2}}{Z_2} + \frac{U_{i_3}}{Z_3}}{\frac{1}{Z_0} + \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$


U_t3=U_i3-U_00;show('Ut3= ',U_t3)
Ut3= 
$$U_{i_3} - \frac{\frac{U_{i_1}}{Z_1} + \frac{U_{i_2}}{Z_2} + \frac{U_{i_3}}{Z_3}}{\frac{1}{Z_0} + \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$

```

---

```
#Fazne (linijske) struje su:
```

```
I_1=U_t1/Z_1; show(I_1)
```

$$U_{i_1} = \frac{\frac{U_{i_1}}{Z_1} + \frac{U_{i_2}}{Z_2} + \frac{U_{i_3}}{Z_3}}{\frac{1}{Z_0} + \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$

```
I_2=U_t2/Z_2; show(I_2)
```

$$U_{i_2} = \frac{\frac{U_{i_1}}{Z_1} + \frac{U_{i_2}}{Z_2} + \frac{U_{i_3}}{Z_3}}{\frac{1}{Z_0} + \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$

```
I_3=U_t3/Z_3; show(I_3)
```

$$U_{i_3} = \frac{\frac{U_{i_1}}{Z_1} + \frac{U_{i_2}}{Z_2} + \frac{U_{i_3}}{Z_3}}{\frac{1}{Z_0} + \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$

```
#Slijedi izracun za zadane podatke
```

```
U_i1=U/sqrt(3); U_i2=U/sqrt(3)*e^(I*(-2*pi/3)); U_i3=U/sqrt(3)*e^(I*\n*2*pi/3); show('Ui1= ',U_i1,'Ui2= ',U_i2,'Ui3= ',U_i3)
```

$$Ui1 = \frac{1}{3}\sqrt{3}U \quad Ui2 = \frac{1}{3}\sqrt{3}U e^{-\frac{2}{3}i\pi} \quad Ui3 = \frac{1}{3}\sqrt{3}U e^{\frac{2}{3}i\pi}$$

```
Z_1=Z; Z_2=Z*e^(-I*pi/6); Z_3=Z*e^(I*pi/6); show('Z1= ',Z_1,'Z2= ',Z_2,\n'Z3= ',Z_3)
```

$$Z1 = Z \quad Z2 = Ze^{(-\frac{1}{6}i\pi)} \quad Z3 = Ze^{(\frac{1}{6}i\pi)}$$

```
U_00=U_00.subs(Z_1=Z,Z_2=Z*e^(-I*pi/6),Z_3=Z*e^(I*pi/6),U_i1=U/sqrt(\n(3), U_i2=U/sqrt(3)*e^(I*(-2*pi/3)),U_i3=U/sqrt(3)*e^(I*2*pi/3))\nshow('U00= ',U_00)
```

$$U00 = \frac{\sqrt{3}U}{3Z\left(\frac{e^{(\frac{1}{6}i\pi)}}{Z} + \frac{e^{(-\frac{1}{6}i\pi)}}{Z} + \frac{1}{Z} + \frac{1}{Z_0}\right)}$$

```
U_00=U_00.simplify_full(); show('U00= ',U_00)
```

$$U00 = \frac{UZ_0}{Z_0(\sqrt{3} + 3) + \sqrt{3}Z}$$

```
#Kako se vidi napon U00 ima samo realnu komponentu
```

```
#Naponi na fazama trosila su:
```

```
U_t1=U_t1.subs(Z_1=Z,Z_2=Z*e^(-I*pi/6),Z_3=Z*e^(I*pi/6),U_i1=U/sqrt(\n(3), U_i2=U/sqrt(3)*e^(I*(-2*pi/3)),U_i3=U/sqrt(3)*e^(I*2*pi/3));\nU_t1=U_t1.simplify_full(); show('Ut1= ',U_t1)
```

```
#Fazni pomak ovog napona je 0:
```

```
show(arg(U_t1).simplify_full())
```

$$Ut1 = \frac{\sqrt{3}UZ + 3UZ_0}{3(Z_0(\sqrt{3} + 1) + Z)}$$

---

```

arctan  $\left(0, \sqrt{3}UZ + 3UZ_0\right) + \arctan \left(0, \frac{Z_0(\sqrt{3}+1) + Z}{\sqrt{2Z_0^2(\sqrt{3}+2) + 2ZZ_0(\sqrt{3}+1) + Z^2}}\right)$ 

U_t2=U_t2.subs(Z_1=Z,Z_2=Z*e^(-I*pi/6),Z_3=Z*e^(I*pi/6),U_i1=U/sqrt\
(3), U_i2=U/sqrt(3)*e^(I*(-2*pi/3)),U_i3=U/sqrt(3)*e^(I*2*pi/3));\
U_t2=U_t2.simplify_full();show('Ut2= ',U_t2)
#Fazni pomak ovog napona je -3*pi/4 rad ili -1[35FFFFD]
show(arg(U_t2).simplify_full())

Ut2=  $-\frac{UZ_0((3i+3)\sqrt{3}+3i+3)+UZ(\sqrt{3}+3i)}{6(Z_0(\sqrt{3}+1)+Z)}$ 
 $\pi+\arctan \left(0, \frac{Z_0(\sqrt{3}+1)+Z}{\sqrt{2Z_0^2(\sqrt{3}+2)+2ZZ_0(\sqrt{3}+1)+Z^2}}\right)+\arctan \left(3UZ_0(\sqrt{3}+1)+3UZ, 3UZ_0(\sqrt{3}+1)\right)$ 

U_t3=U_t3.subs(Z_1=Z,Z_2=Z*e^(-I*pi/6),Z_3=Z*e^(I*pi/6),U_i1=U/sqrt\
(3), U_i2=U/sqrt(3)*e^(I*(-2*pi/3)),U_i3=U/sqrt(3)*e^(I*2*pi/3));\
U_t3=U_t3.simplify_full();show('Ut3= ',U_t3)
#Fazni pomak ovog napona je 3*pi/4 rad ili +1[35FFFFD]
show(arg(U_t3).simplify_full())

Ut3=  $-\frac{UZ(\sqrt{3}-3i)-UZ_0((3i-3)\sqrt{3}+3i-3)}{6(Z_0(\sqrt{3}+1)+Z)}$ 
 $\pi+\arctan \left(0, \frac{Z_0(\sqrt{3}+1)+Z}{\sqrt{2Z_0^2(\sqrt{3}+2)+2ZZ_0(\sqrt{3}+1)+Z^2}}\right)-\arctan \left(3UZ_0(\sqrt{3}+1)+3UZ, 3UZ_0(\sqrt{3}+1)\right)$ 

#Fazne (linijske) struje su
I_1=U_t1/Z_1;I_1=I_1.subs(Z_1=Z);I_1=I_1.simplify_full();show('I1= '\
,I_1)
# a fazni je pomak strtuje:
show(arg(U_t1).simplify_full()-arg(Z_1).simplify_full())

I1=  $\frac{\sqrt{3}UZ+3UZ_0}{3(ZZ_0(\sqrt{3}+1)+Z^2)}$ 
 $\arctan \left(0, \sqrt{3}UZ+3UZ_0\right)-\arctan(0,Z)+\arctan \left(0, \frac{Z_0(\sqrt{3}+1)+Z}{\sqrt{2Z_0^2(\sqrt{3}+2)+2ZZ_0(\sqrt{3}+1)+Z^2}}\right)$ 

I_2=U_t2/Z_2;I_2=I_2.subs(Z_2=Z*e^(-I*pi/6));I_2=I_2.simplify_full()\ 
;show('I2= ',I_2)
# a fazni je pomak strtuje:
show(arg(U_t2).simplify_full()-arg(Z_2).simplify_full())

I2=  $-\frac{UZ_0(3i\sqrt{3}+6i+3)+2i\sqrt{3}UZ}{6(ZZ_0(\sqrt{3}+1)+Z^2)}$ 
 $\frac{7}{6}\pi-\arctan(0,Z)+\arctan \left(0, \frac{Z_0(\sqrt{3}+1)+Z}{\sqrt{2Z_0^2(\sqrt{3}+2)+2ZZ_0(\sqrt{3}+1)+Z^2}}\right)+\arctan \left(3UZ_0(\sqrt{3}+1)+3UZ, 3UZ_0(\sqrt{3}+1)\right)$ 

```

---

```

I_3=U_t3/Z_3;I_3=I_3.subs(Z_2=Z*e^(I*pi/6));I_3=I_3.simplify_full();\
    show('I3= ',I_3)
# a fazni je pomak strtuje:
show(arg(U_t3).simplify_full()-arg(Z_3).simplify_full())
I3= 
$$\frac{U Z_0(3i\sqrt{3} + 6i - 3) + 2i\sqrt{3}UZ}{6(ZZ_0(\sqrt{3} + 1) + Z^2)}$$


$$\frac{5}{6}\pi - \arctan(0, Z) + \arctan\left(0, \frac{Z_0(\sqrt{3} + 1) + Z}{\sqrt{2}Z_0^2(\sqrt{3} + 2) + 2ZZ_0(\sqrt{3} + 1) + Z^2}\right) - \arctan\left(3UZ_0(\sqrt{3} + 1) + 3UZ\right)$$


#Slijedi izracun za zadane numericke podatke:
U_00=(U_00.subs(U=250,Z=10,Z_0=1)).n();U_00
11.3365528836565

U_t1=(U_t1.subs(U=250,Z=10,Z_0=1)).n();U_t1
133.001014413750

U_t2=(U_t2.subs(U=250,Z=10,Z_0=1)).n();U_t2
-83.5053365323598 - 125.0000000000000*I

U_t3=(U_t3.subs(U=250,Z=10,Z_0=1)).n();U_t3
-83.5053365323598 + 125.0000000000000*I

I_1=(I_1.subs(U=250,Z=10,Z_0=1)).n();I_1
13.3001014413750

I_2=(I_2.subs(U=250,Z=10,Z_0=1)).n();I_2
-0.981774278859229 - 15.0005843739235*I

I_3=(I_3.subs(U=250,Z=10,Z_0=1)).n();I_3
-0.981774278859229 + 15.0005843739235*I

S_1=U_t1*conjugate(I_1);S_1
1768.92698350865

S_2=U_t2*conjugate(I_2);S_2
1957.05643829539 - 1129.90706146913*I

S_3=U_t3*conjugate(I_3);S_3
1957.05643829539 + 1129.90706146913*I

S_uk=S_1+S_2+S_3;S_uk
5683.03986009943

```